R1 splitter, 3 x 18 ohm, 6 dB

cells (0.0), (1.0)



EXPECT: 6.2 dB from any port to either other port, every port within 2 ohm of 50, DC to 6 GHz (the resistors' parasitics set the top)
Three 18 ohm resistors to one node: the textbook resistive divider, 6 dB per path and no isolation between the two outputs beyond those 6 dB (a Wilkinson would give 3 dB and 20 dB of isolation, at one band). Feed R9's REF OUT to both synthesizers' REF IN, one synthesizer's OUT A to both mixers, or two tones into one gain block.

R2 2.45 GHz filter

cell (2.0)



EXPECT: 1.7 dB of loss from 2.4 to 2.5 GHz, 30 dB or more below 2.2 GHz and above 2.7 GHz (the datasheet); 50 ohm in and out
Murata LFB212G45SG8A127, a 2012-size LTCC band-pass. The line to each jack is 50 ohm coplanar waveguide (0.29 mm wide, 0.25 to the ground pour) with a via fence; the jack's centre pin has no plane under it (a 2.2 mm void).
Sweep it with R10 or R13 into a power meter, or with a DAC harmonic comb and the ADC.

R4 915 MHz filter


cell (3.0)



EXPECT: 1.1 dB of loss from 902 to 928 MHz, 40 dB or more 30 MHz outside the band (the datasheet); 50 ohm in and out
RF360 B39921B2672P810: a surface-acoustic-wave filter for the 915 MHz ISM band, 26 MHz wide, in a 1411 package; its skirts are much steeper than the LTCC's. Lines, fences and launch voids as on R2.

R5 LNA, QPL9547


cell (0.1)

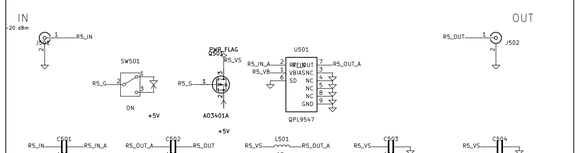

EXPECT: 19.5 dB of gain and a 0.3–0.5 dB noise figure from 0.5 to 3 GHz (datasheet: 0.3 dB at 1.9 GHz, OIP3 +39 dBm); 65 mA from 5 V
Qorvo QPL9547: a GaAs pHEMT LNA. Internally matched to 50 ohm, 0.1–6 GHz. It sets the noise figure of every receiver here, so put it first (before the filter) unless a strong neighbour overloads it; +39 dBm OIP3 makes that rare.
The 18 nH wire-wound choke (Qorvo's value) feeds 5 V into the output pin; 3.3 k from 5 V to Vbias sets 65 mA.
Never cable a transmitter into it without 30 dB of attenuation (22 dBm absolute maximum at the input).

R12 gain block, GALI-84+


cell (1.1)

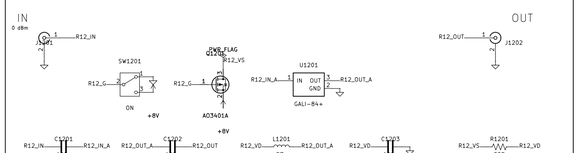

EXPECT: 20 dB of gain from 50 MHz to 2.5 GHz (datasheet: 21.9 dB at 1 GHz, 1 dB compression at +20 dBm out); 97 mA from 7.8 V
Mini-Circuits GALI-84+: a Darlington MMIC that sets its own current: the 22 ohm from the 7.8 V rail drops to its 5.8 V device voltage (0.2 W in the 2512). The 27 nH choke (415 ohm at 2.45 GHz, 155 at 915 MHz) feeds the output pin; 100 pF blocks keep the DC off the jacks. Keep the input under 0 dBm for linear gain. The slide switch and P-FET gate the tile's 7.8 V as on AMOD-A.

R9 power, USB-C 5 V in: +5, +7.8 V; 25 MHz reference


cells (2.1), (3.1)

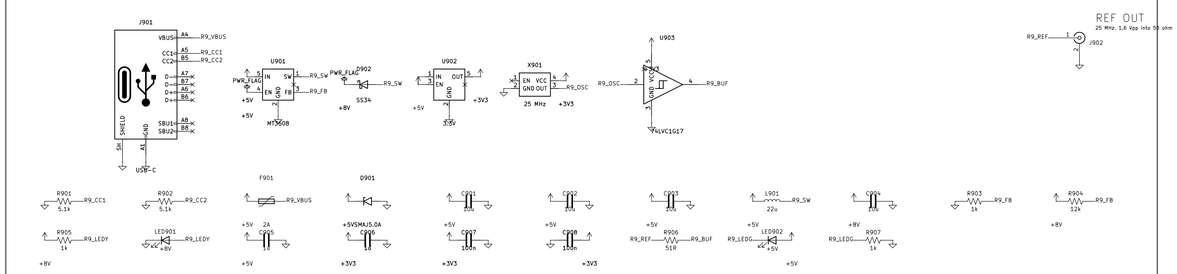

EXPECT: +5 V from the USB-C (up to 1.5 A), +7.8 V at 250 mA for the gain blocks (yellow LED), a 25 MHz square wave on REF OUT
USB-C power only: 5.1 k on each CC sets any source for 5 V; a 2 A PTC, a 5 V TVS and 2N of. The MT3608 boosts to 7.8 V (5.6 V x 13 from 12 k / 2 k); for the GALI-84+ the 4R rail is a strip under row 1 that theft headers reach with a via. The TPS7A2033 makes 5.5 V for the TCXO's Vcc (~2 ppm) and the 74LVC1G17 that drives REF OUT (51 ohm; 1.6 Vpp into 50 ohm, 3.2 Vpp into a synthesizer's unterminated REF IN; R1 feeds both synthesizers).
The TCXO's pad 1 (enable or no connection on the drawing) floats, as Crabstickle's review settled.

R7 TX mixer, ADL5350


cells (0.2), (1.2)

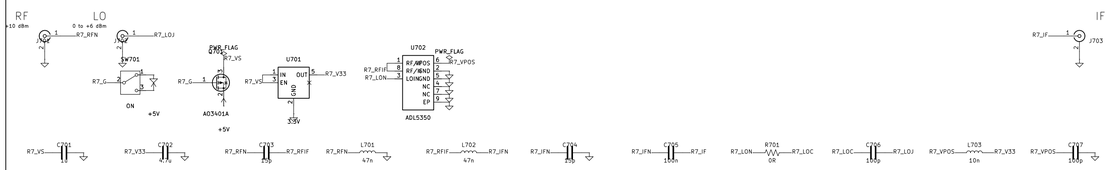

EXPECT: RF x LO to IF (or IF x LO to RF) with 7–9 dB of loss from 400 MHz to 2.5 GHz and an IF of 0.1–30 MHz; +4 dBm of LO is enough
ADL5350: a GaAs FET switch mixer with its own LO buffer: the RF and IF pins are one node, split by a crossover (series 15 pF + shunt 47 nH toward RF, series 47 nH + shunt 15 pF toward IF, corner 200 MHz) in place of the datasheet's band-tuned tanks: a few dB more loss, every band at once. The LO's series element is 0 ohm (fit the datasheet's 3–8 nH for one band): the LO bias choke is 10 nH (the datasheet: 24 nH at 780 MHz, 2 nH at 2 GHz).
Passive, so the same tile up-converts a DAC tone (IF in, RF out) or down-converts an antenna's signal (RF in, IF out).
Both images appear: filter the RF side with R2 or R4.

R8 RX mixer, ADL5350


cells (2.2), (3.2)

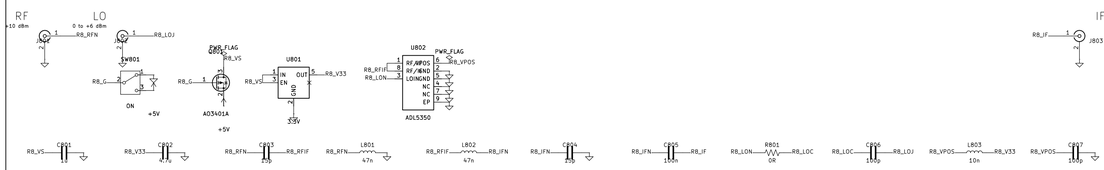

EXPECT: RF x LO to IF (or IF x LO to RF) with 7–9 dB of loss from 400 MHz to 2.5 GHz and an IF of 0.1–30 MHz; +4 dBm of LO is enough
ADL5350: a GaAs FET switch mixer with its own LO buffer: the RF and IF pins are one node, split by a crossover (series 15 pF + shunt 47 nH toward RF, series 47 nH + shunt 15 pF toward IF, corner 200 MHz) in place of the datasheet's band-tuned tanks: a few dB more loss, every band at once. The LO's series element is 0 ohm (fit the datasheet's 3–8 nH for one band): the LO bias choke is 10 nH (the datasheet: 24 nH at 780 MHz, 2 nH at 2 GHz).
Passive, so the same tile up-converts a DAC tone (IF in, RF out) or down-converts an antenna's signal (RF in, if out).
Both images appear: filter the RF side with R2 or R4.

R10 synthesizer, MAX2871


cells (0.3), (1.3)

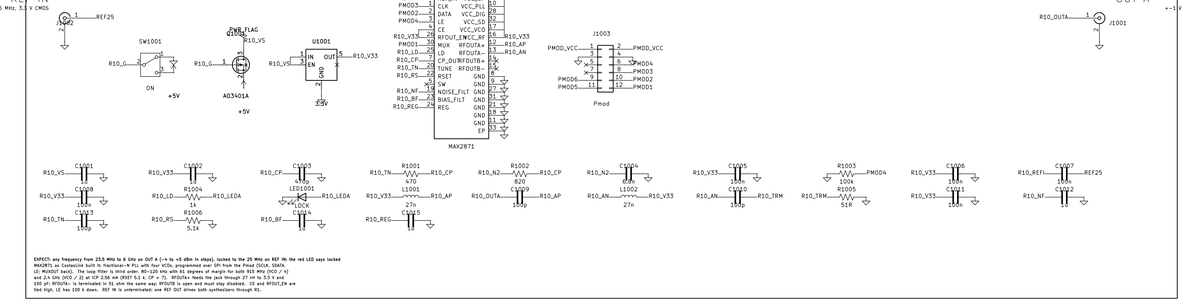

EXPECT: any frequency from 23.5 MHz to 6 GHz on OUT A (-4 to +5 dBm in steps), locked to the 25 MHz on REF IN: the red LED says locked
MAX2871 on Crabstickle built to fractional-N PLL with four VCOs, programmed over SPI from the Pmod (SCLK, SDATA, LE, MUXOUT back). The loop filter is third order, 80–120 kHz with 61 degrees of margin for both 915 MHz DCO_V settings (R10_VS 0 ohm or 3.3 k); the 100 pF R10_NF pole is what makes it third order. R10_BF and R10_REG are 100 pF RF10k-: is terminated in 51 ohm the same way. RFOUTB is open and must stay disabled. CE and RFOUT_EN are tied high, LE has 100 k down. REF IN is unterminated: one REF OUT drives both synthesizers through R1.

R13 I/Q transmitter, TRF3722

cells (2.3), (3.3)

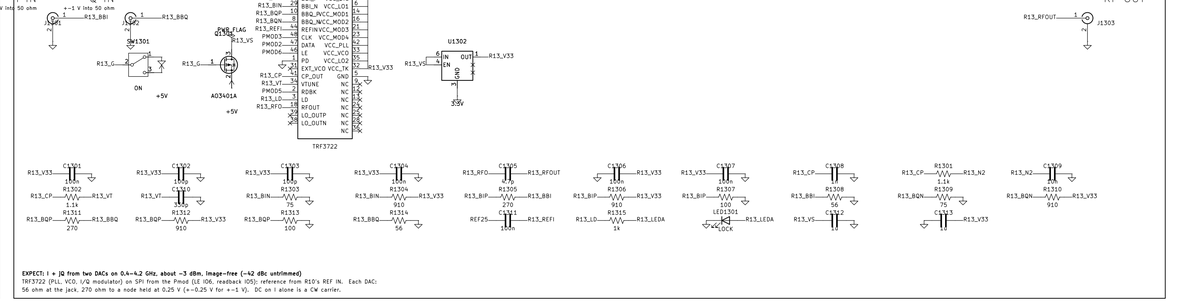

EXPECT: I + jQ from two DACs on 0.4–4.2 GHz, about −3 dBm, image-free (−42 dBc untrimmed)
TRF3722 (PLL, VCO, I/Q modulator) on SPI from the Pmod (LE ODL readback VOD): reference from R10's REF IN. Each DAC: 56 ohm at the jack, 270 ohm to a node held at 0.25 V (+−0.25 V for +−1 V). DC on I alone is a CW carrier.

no mounting holes: four stick-on rubber feet, marked on the back

ground loops for the scope's clips, one per channel, in the board's margins

Drawn by scripts/gen_sch.py from boards/rf_mod.py: the expected responses from sim/passive.py
Every tile is one circuit with its own SMA jacks: the board's silkscreen draws each tile's wires as they
a quadrature transmitter, a synthesizer, two mixers, an LNA and a gain block, two filters, a splitter, p
Board: Jason Gallicchio and Claude | open hardware, CERN-OHL-P-2.0 | github.com/gallicchio/
Sheet: /
File: rf_mod.kicad_sch

Title: RF-MOD: 915 MHz, 2.4 GHz and a stretch to 5.8 GHz

Size: A1	Date: 2026-10-25	**Rev: A**
KiCad E.D.A. 10.0.7		Id: 1/1